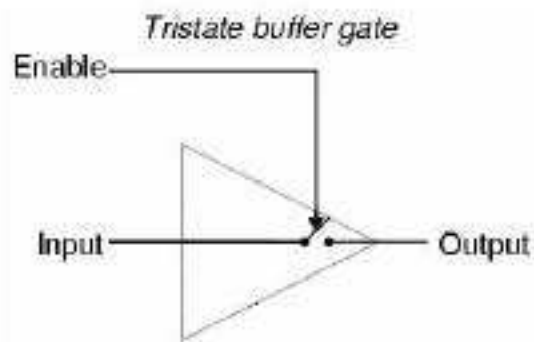


- How can multiple devices share a single set of wires?



$Enable = 1 \Rightarrow Output = Input$

$Enable = 0 \Rightarrow Output = Z$

$Z \Leftrightarrow \underline{DISCONNECTED}$

