

### A) Problem description

y is 1 if a is to 1, or b and c are 1. z is 1 if b or c is to 1, but not both, or if all are 1.

### B) Truth table

Inputs			Outputs	
a	b	c	y	z
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

### C) Output equations

$$y = a'bc + ab'c' + ab'c + abc' + abc$$

$$z = a'b'c + a'bc' + ab'c + abc' + abc$$

### D) Minimized output equations

y	bc			
a	00	01	11	10
0	0	0	1	0
1	1	1	1	1

$$y = a + bc$$

z	bc			
a	00	01	11	10
0	0	1	0	1
1	0	1	1	1

$$z = ab + b'c + bc'$$

### E) Logic Gates

