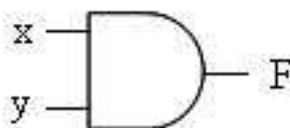





$F = x$   
Driver

| x | F |
|---|---|
| 0 | 0 |
| 1 | 1 |




$F = x y$   
AND

| x | y | F |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

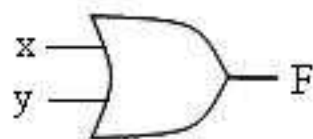


$F = x + y$   
OR

| x | y | F |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

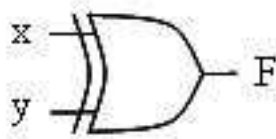


$F = x \oplus y$   
XOR

| x | y | F |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

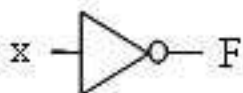


$F = x'$   
Inverter

| x | F |
|---|---|
| 0 | 1 |
| 1 | 0 |

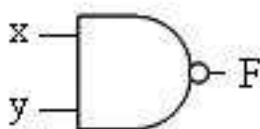


$F = (x y)'$   
NAND

| x | y | F |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

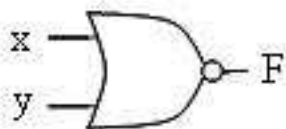

$F = (x+y)'$   
NOR

| x | y | F |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

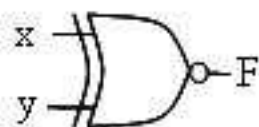

$F = x \odot y$   
XNOR

| x | y | F |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |