

# VERILOG TUTORIAL

## **VLSI II**

**E. Özgür ATES**

# Outline

- Introduction
- Language elements
- Gate-level modeling
- Data-flow modeling
- Behavioral modeling
- Modeling examples
- Simulation and test bench

# Hardware Description Language

- Have high-level language constructs to describe the functionality and connectivity of the circuit
- Can describe a design at some levels of abstraction
  - Behavioral (Algorithmic, RTL), Structural (Gate-level), Switch (For example, an HDL might describe the layout of the wires, resistors and transistors on an Integrated Circuit (IC) chip, i. e. the switch level. Or, it might describe the logical gates and flip flops in a digital system, i. e., the gate level. An even higher level describes the registers and the transfers of vectors of information between registers. This is called the Register Transfer Level (RTL). Verilog supports all of these levels.)

# Hardware Description Language

- A design's abstraction levels

- **Behavioral**

**Algorithmic:** A model that implements a design algorithm in high-level language constructs

**RTL:** A model that describes the flow of data between registers and how a design processes that data

- **Gate-level:** A model that describes the logic gates and the connections between logic gates in a design

- **Switch-level:** A model that describes the transistors and storage nodes in a device and the connections between them

# Verilog Hardware Description Language


- Verilog was started initially as a proprietary hardware modeling language by Gateway Design Automation Inc. around 1984. It is rumored that the original language was designed by taking features from the most popular HDL language of the time, called HiLo, as well as from traditional computer languages such as C.
- Verilog simulator was first used beginning in 1985 and was extended substantially through 1987. The implementation was the Verilog simulator sold by Gateway. The first major extension was Verilog-XL, which added a few features and implemented the infamous "XL algorithm" which was a very efficient method for doing gate-level simulation.

# Verilog Hardware Description Language

- The time was late 1990. Cadence Design System, whose primary product at that time included Thin film process simulator, decided to acquire Gateway Automation System. Along with other Gateway products, Cadence now became the owner of the Verilog language.
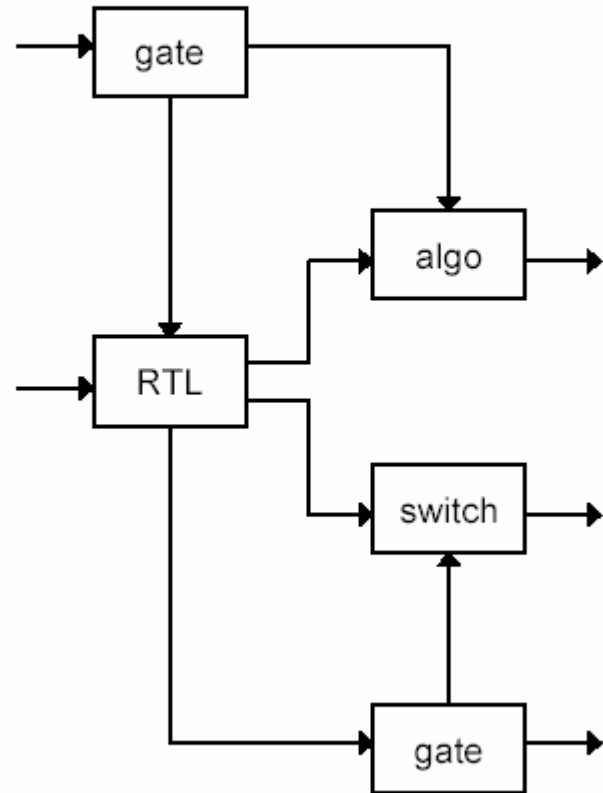
# What is Verilog HDL ?

- Hardware description language
- Mixed level modeling
  - Behavioral
    - Algorithmic
    - Register transfer
  - Structural
    - Gate
    - Switch
- Single language for design and simulation
- Built-in primitives and logic functions
- User-defined primitives
- Built-in data types
- High-level programming constructs



# Hardware Description Language

**Hardware Description Languages describe the architecture and behavior of discrete and integrated electronic systems. Modern HDLs and their associated simulators are very powerful tools for integrated circuit designers.**

**Main reasons of important role of HDL in modern design methodology:**

- Design functionality can be verified early in the design process. Design simulation at this higher level, before implementation at the gate level, allows you to evaluate architectural and design decisions.**



# Hardware Description Language


- **Coupling HDL Compiler with logic synthesis tools, you can automatically convert an HDL description to a gate-level implementation in a target technology.**
- **HDL descriptions provide technology-independent documentation of a design and its functionality. Since the initial HDL design description is technology-independent, you can use it again to generate the design in a different technology, without having to translate from the original technology.**

# Hardware Description Language

**Verilog digital logic simulator tools allow you to perform the following tasks in the design process without building a hardware prototype:**

- **Determine the feasibility of new design ideas**
- **Try more than one approach to a design problem**
- **Verify functionality**
- **Identify design problems**

## *HDL Compiler and Design Compiler*

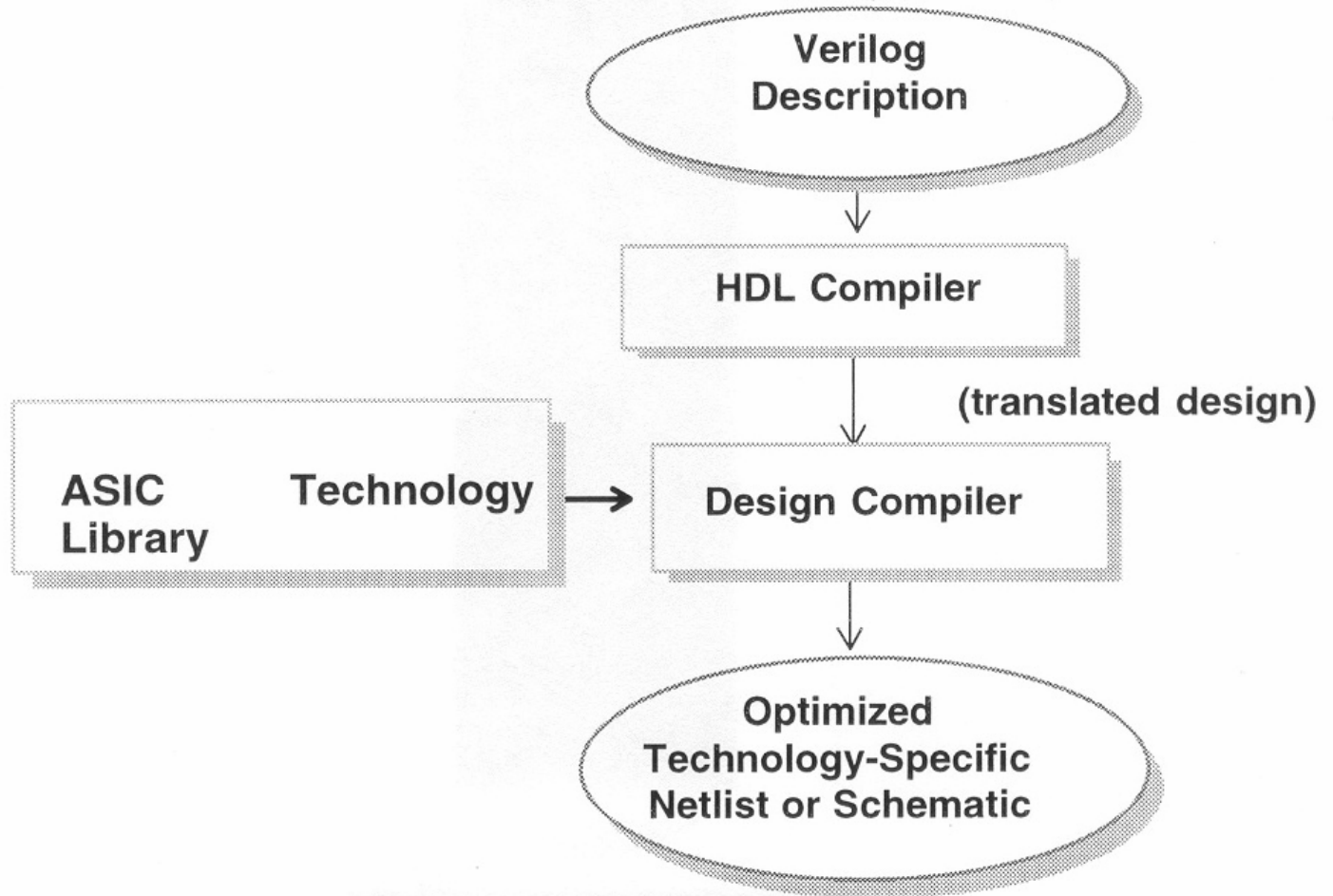

# Basic Unit -- Module

- Modules communicate externally with input, output and bi-directional ports
- A module can be instantiated in another module

**module** module\_name (port\_list);

*declarations:*

port declaration (input, output, inout, ...)

data type declaration (reg, wire, parameter, ...)

task and function declaration

*statements:*

initial block

always block



module instantiation

gate instantiation

UDP instantiation

continuous assignment

**endmodule**

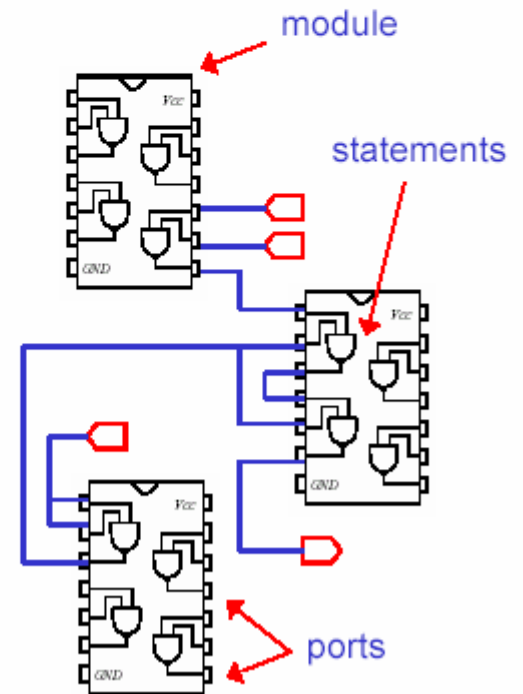 

# An Example

```
module FA_MIX (A, B, CIN, SUM, COUT);  
  input A,B,CIN;  
  output SUM, COUT;  
  reg COUT;  
  reg T1, T2, T3;  
  wire S1;  
  
  xor X1 (S1, A, B); // Gate instantiation.  
  
  always @ (A or B or CIN) // Always Block  
  begin  
    T1 = A & CIN;  
    T2 = B & CIN;  
    T3 = A & B;  
    COUT = (T1 | T2 | T3);  
  END  
  assign SUM = S1 ^ CIN; // Continuous assignment  
endmodule
```

# Structural Hierarchy Description Style


- Direct instantiation and connection of models from a separate calling model
  - Form the structural hierarchy of a design
- A module may be declared anywhere in a design relative to where it is called
- Signals in the higher “calling” model are connected to signals in the lower “called” model by either:
  - Named association
  - Positional association

# Structural Hierarchy Description Style

- Example: (Full Adder)

```
module FULL_ADD (A, B, CIN, SUM, COUT);  
  input A, B, CIN;  
  output SUM, COUT;  
  wire NET1, NET2, NET3;  
  
  HA U1(NET1, NET2, B, CIN); /* positional association */  
  HA U2(.S(SUM), .CO(NET3), .A(A), .B(NET1)); /* named */  
  OR2 U3(COUT, NET2, NET3);  
endmodule
```

← instance name

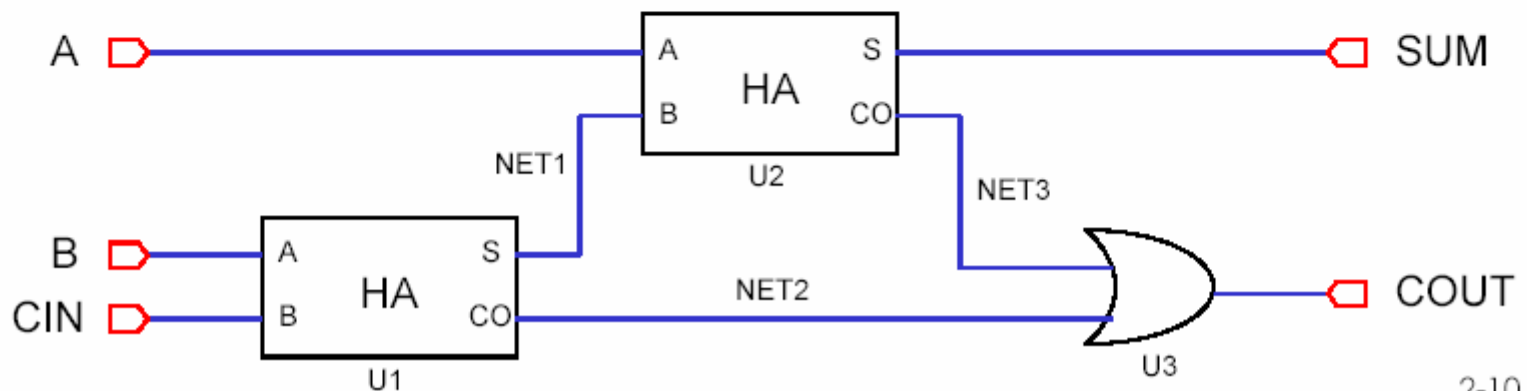

# Lexical Conventions

- Verilog is a free-format language
  - Like C language
- White space (blank, tab, newline) can be used freely
- Verilog is a **case-sensitive** language
- Identifiers
  - User-provided names for Verilog objects in the descriptions
  - Legal characters are “a-z”, “A-Z”, “0-9”, “\_”, and “\$”
    - First character has to be a letter or an “\_”
  - Example: Count, \_R2D2, FIVE\$
- Keywords
  - Predefined identifiers to define the language constructs
  - All keywords are defined in lower case
  - Cannot be used as identifiers
  - Example: **initial**, **assign**, **module**



# Lexical Conventions

- Comments: two forms

- `/*` First form: can  
extend over many  
lines `*/`

- `//` Second form: ends at the end of this line

- Strings

- Enclosed in double quotes and must be specified in one line

- “Sequence of characters”

- Accept C-like escape character

- `\n` = newline

- `\t` = tab

- `\\` = backslash

- `\` = quote mark (“)

- `%%` = % sign

# Value Set

- 0: logic-0 / FALSE
- 1: logic-1 / TRUE
- x: unknown / don't care, can be 0, 1 or z.
- z: high-impedance

# Number Representation

<size><base format><number>

549 // decimal number

'h 8FF // hex number

'o765 // octal number

4'b11 // 4-bit binary number 0011

3'b10x // 3-bit binary number with least significant bit unknown

5'd3 // 5-bit decimal number

-4'b11 // 4-bit two's complement of 0011 or 1101

# Data Types

- Nets
  - Connects between structural elements
  - Values come from its drivers
    - Continuous assignment
    - Module or gate instantiation
  - If no drivers are connected to net, default value is Z
- Registers
  - Represent abstract data storage elements
  - Manipulated within procedural blocks
  - The value in a register is saved until it is overridden
  - Default value is X

# Net Types

- **wire, tri**: standard net
- **wor, trior**: wired-or net
- **wand, triand**: wired-and net
- **triereg**: capacitive
  - If all drivers at z, previous value is retained
- **tri1**: pull up (if no driver, 1)
- **tri0**: pull down (if no driver, 0)
- **supply0**: ground
- **supply1**: power
- A net that is not declared defaults to a 1-bit wire
  - wire reset;
  - wor [7:0] DBUS;
  - supply0 GND;

# Register Types

- **reg**: any size, unsigned
- **integer**: 32-bit signed (2's complement)
- **time**: 64-bit unsigned
- **real, realtime**: 64-bit real number
  - Defaults to an initial value of 0
- **Examples**:
  - reg CNT;
  - reg [31:0] SAT;
  - integer A, B, C; // 32-bit
  - real SWING;
  - realtime CURR\_TIME;
  - time EVENT;

# Outline


- Introduction
- Language elements
- Gate-level modeling
- Data-flow modeling
- Behavioral modeling
- Modeling examples
- Simulation and test bench

# Primitive Gates

- The following gates are built-in types in the simulator
- **and, nand, nor, or, xor, xnor**
  - First terminal is output, followed by inputs  
`and a1 (out1, in1, in2);`  
`nand a2 (out2, in21, in22, in23, in24);`
- **buf, not**
  - One or more outputs first, followed by one input  
`not N1 (OUT1, OUT2, OUT3, OUT4, INA);`  
`buf B1 (BO1, BIN);`
- **bufif0, bufif1, notif0, notif1**: three-state drivers
  - Output terminal first, then input, then control  
`bufif1 BF1 (OUTA, INA, CTRLA);`
- **pullup, pulldown**
  - Put 1 or 0 on all terminals  
`pullup PUP (PWRA, PWRB, PWRC);`
- Instance names are optional  
ex: `not (QBAR, Q)`



# Example

 

4 X 1 multiplexer circuit

```
module MUX4x1 (Z, D0, D1, D2, D3, S0, S1);  
  output Z;  
  input D0, D1, D2, D3, S0, S1;  
  
  and (T0, D0, S0BAR, S1BAR),  
      (T1, D1, S0BAR, S1),  
      (T2, D2, S0, S1BAR),  
      (T3, D3, S0, S1);  
  
  not (S0BAR, S0),  
      (S1BAR, S1);  
  
  nor (Z, T0, T1, T2, T3);  
endmodule
```

# Outline

- Introduction
- Language elements
- Gate-level modeling
- Data-flow modeling
- Behavioral modeling
- Modeling examples
- Simulation and test bench

# Data-Flow Description Style

- Models behavior of combinational logic
- Assign a value to a net using *continuous assignment*
- Examples:

```
wire [3:0] Z, PRESET, CLEAR;  
assign Z = PRESET & CLEAR;  
  
wire COUT, CIN;  
wire [3:0] SUM, A, B;  
assign {COUT, SUM} = A + B + CIN;
```
- Left-hand side (target) expression can be a:
  - Single net (ex: Z)
  - Part-select (ex: SUM[2:0])
  - Bit-select (ex: Z[1])
  - Concatenation of both (ex: {COUT, SUM[3:0]})
- Expression on right-hand side is evaluated whenever any operand value changes

# Delays

- Delay between assignment of right-hand side to left-hand side
  - `assign #6 ASK = QUIET || LATE; //Continuous delay`
- Net delay
  - `wire #5 ARB;`
  - `// Any change to ARB is delayed 5 time units before it takes effect`
- If value changes before it has a chance to propagate, latest value change will be applied
  - Inertial delay

# Operators

Arithmetic Operators	+, -, *, /, %
Relational Operators	<, <=, >, >=
Logical Equality Operators	==, !=
Case Equality Operators	===, !==
Logical Operators	!, &&,
Bit-Wise Operators	~, &,  , ^(xor), ~^(xnor)
Unary Reduction Operators	&, ~&,  , ~ , ^, ~^
Shift Operators	>>, <<
Conditional Operators	? :
Concatenation Operator	{ }
Replication Operator	{ { } }

# Outline

- Introduction
- Language elements
- Gate-level modeling
- Data-flow modeling
- Behavioral modeling
- Modeling examples
- Simulation and test bench

# Behavioral Modeling

- Procedural blocks:
  - **initial block**: executes only once
  - **always block**: executes in a loop
- Block execution is triggered based on user-specified conditions
  - **always @ (posedge clk) .....**
- All procedural blocks are automatically activated at time 0
- All procedural blocks are executed **concurrently**
- **reg** is the main data type that is manipulated within a procedural block
  - It holds its value until assigned a new value

# Parameter Statement

The parameter statement allows the designer to give a constant a name. Typical uses are to specify width of registers and delays. For example, the following allows the designer to parameterized the declarations of a model.

```
parameter byte_size = 8;
```

```
reg [byte_size - 1:0] A, B;
```



# Initial Statement

- Executes only once at the beginning of simulation  
initial  
*statements*
- Used for initialization and waveform generation

//Initialization:

**reg** [7:0] RAM[0:1023];

**reg** RIB\_REG;

**initial**

**begin**

**integer** INX;

RIB\_REG = 0;

**for** (INX = 0; INX < 1024; INX = INX + 1)

RAM[INX] = 0;

**end**

group  
multiple  
statements

# Always Statement

- Executes continuously; must be used with some form of timing control

```
always (timing_control)  
    statements
```

```
always  
    CLK = ~CLK  
    // Will loop indefinitely
```

- Four forms of event expressions are often used
  - An **OR** of several identifiers (comb/seq logic)
  - The rising edge of a identifier (for clock signal of a register)
  - The falling edge of a identifier (for clock signal of a register)
  - Delay control (for waveform generator)
- Any number of *initial* and *always* statements may appear within a module
- Initial and always statements are all executed in parallel

# Truth Table to Verilog

```
module COMB(A, B, Y1, Y2);  
  input A, B;  
  output Y1, Y2;  
  reg Y1, Y2;  
  
  always @(A or B)  
  begin  
    case ({A, B})  
      2'b 00 : begin Y1=1; Y2=0; end  
      2'b 01 : begin Y1=1; Y2=0; end  
      2'b 10 : begin Y1=1; Y2=0; end  
      2'b 11 : begin Y1=0; Y2=1; end  
    endcase  
  end  
  
endmodule
```

Any value changes of A or B  
will trigger this block



A	B	Y1	Y2
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	1

# Other Examples

```
module example (D, CURRENT_STATE, Q, NEXT_STATE);
```

```
    input D, CURRENT_STATE;  
    output Q, NEXT_STATE;  
    reg CLK, Q, NEXT_STATE;
```

delay-controlled always block  
clock period = 10

```
    always #5 CLK = ~CLK;
```

activated when CLK has  
a 0 -> 1 transition

```
    always @(posedge CLK)
```

```
    begin
```

```
        Q = D;
```

```
    end
```

activated when CLK has  
a 1 -> 0 transition

```
    always @(negedge CLK)
```

```
    begin
```

```
        NEXT_STATE = CURRENT_STATE;
```

```
    end
```

```
endmodule
```

# Procedural Assignments

- The assignment statements that can be used inside an *always* or *initial* block
- The target must be a register or integer type
- The following forms are allowed as a target
  - Register variables
  - Bit-select of register variables (ex: A[3])
  - Part-select of register variables (ex: A[4:2])
  - Concatenations of above (ex: {A, B[3:0]})
  - Integers

```
always @(posedge CLK) begin
    B = A;
    C = B;
end
```

# Conditional Statements

- *if and else if* statements

```
if (expression)
    statements
{ else if (expression)
    statements      }
[ else
    statements      ]
```

```
if (total < 60) begin
    grade = C;
    total_C = total_C + 1;
end
else if (sum < 75) begin
    grade = B;
    total_B = total_B + 1;
end
else grade = A;
```

- *case* statement

```
case (case_expression)
    case_item_expression
    {, case_item_expression } :
    statements
    .....
    [ default: statements ]
endcase
```

```
case (OP_CODE)
    2`b10:    Z = A + B;
    2`b11:    Z = A - B;
    2`b01:    Z = A * B;
    2`b00:    Z = A / B;
    default:  Z = 2`bx;
endcase
```

# Loop Statements

- Four loop statements are supported
  - The *for* loop
  - The *while* loop
  - The *repeat* loop
  - The *forever* loop
- The syntax of loop statements is very similar to that in C language
- Most of the loop statements are not synthesizable in current commercial synthesizers

```
for(i = 0; i < 10; i = i + 1)
begin
    $display("i= %0d", i);
end
```

```
i = 0;
while(i < 10)
begin
    $display("i= %0d", i);
    i = i + 1;
end
```

```
repeat (5)
begin
    $display("i= %0d", i);
    i = i + 1;
end
```




# Outline

- Introduction
- Language elements
- Gate-level modeling
- Data-flow modeling
- Behavioral modeling
- Modeling examples
- Simulation and test benches

# Combinational Circuit Design

- Outputs are functions of inputs

 

- The sensitivity list **must** include all inputs

always @ (a or b or c)

$f = a \& \sim c \mid b \& c ;$

- Wrong example:

always @ (a or b)


$f = a \& \sim c \mid b \& c ;$

- The changes of c will not change the output immediately
- May cause functional mismatch in the synthesized circuits
  - Unlike simulation, synthesizers will skip the sensitivity list and deal with the following statements directly

# An Example: Multiplexer

- Continuous assignment

```
module mux2_1(out,a,b,sel);  
    output out;  
    input a,b,sel;  
    assign out = (a&~sel) |  
                (b&sel);  
endmodule
```

 

- RTL modeling

```
module mux2_1(out,a,b,sel);  
    output out;  
    input a,b,sel;  
    reg out;  
    always @(a or b or sel)  
        if (sel)  
            out = b;  
        else  
            out = a;  
endmodule
```

# Multiplexer Example

## Where is the register?

- The synthesis tool figures out that this is a combinational circuit. Therefore, it does not need a register.

## How does it figure out that this is combinational?

- The output is only a function of the inputs (and not of previous values)
- Anytime an input changes, the output is re-evaluated.

# Combinational Design Error

```
module blah (f, g, a, b, c);  
  output  f, g;  
  input   a, b, c;  
  reg     f, g;  
  
  always @ (a or b or c)  
    if (a == 1)  
      f = b;  
    else  
      g = c;  
  
endmodule
```

This says: as long as  $a==1$ , then  $f$  follows  $b$ . (i.e. when  $b$  changes, so does  $f$ .) But, when  $a==0$ ,  $f$  remembers the old value of  $b$ .


Combinational circuits don't remember anything!

What's wrong?


$f$  doesn't appear in *every* control path in the always block (neither does  $g$ ).
 
# IF-ELSE Statement

```
if (A(0) == 0 and A(1) == 0) then  
    B = C;  
else if (A(0) == 1 and A(1) == 0) then  
    B = D;  
else if (A(0) == 0 and A(1) == 1) then  
    B = E;  
else  
    B = F;  
end if;
```



# Case Statement

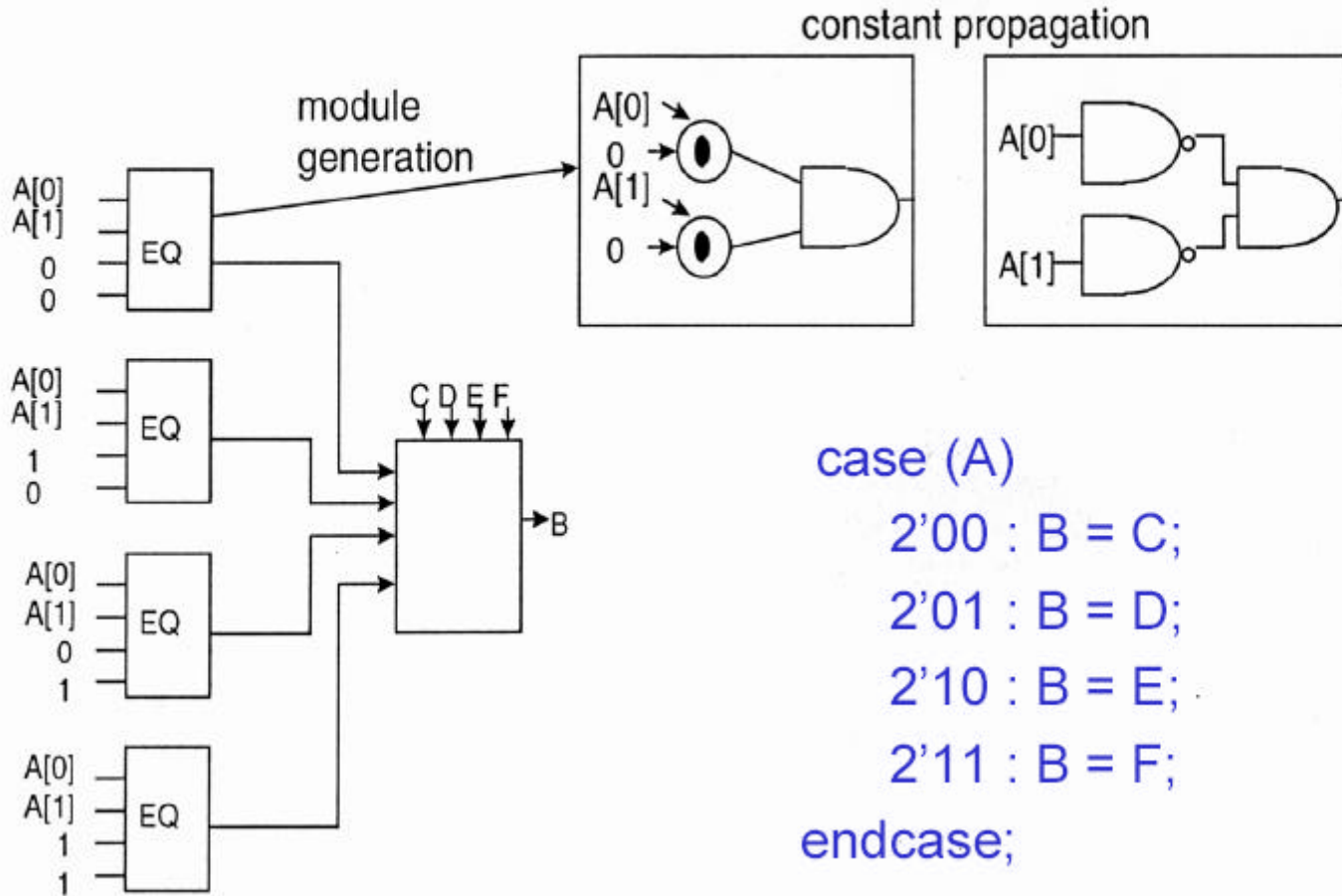


# Tri-State Buffers

- Two popular ways to describe a tri-state buffer

```
// continuous assignment  
assign out = (sela) ? a : 1'bz ;
```
 
```
// RTL modeling  
always @(selb or b)  
  if (selb)  
    out = b ;  
  else  
    out = 1'bz;
```





# Tasks and Functions

**Tasks** are like procedures in other programming languages, e. g. they may have zero or more arguments and do not return a value. Functions act like function subprograms in other languages. Except:

1. A Verilog function must execute during one simulation time unit. That is, no time controlling statements, i. e., no delay control (#), event control (@) or **wait** statements, allowed. A task may contain controlled statements.
2. A Verilog function can *not* invoke (call, enable) a task; whereas a task may call other tasks and functions.

# Tasks and Functions

The definition of a task is the following:

```
task <task name>; // Notice: no parameter list or ()s
  <argument ports>
  <declarations>
  <statements>
endtask
```

An invocation of a task is of the following form:

```
<name of task> (<port list>);
```

## Tasks and Functions

where **<port list>** is a list of expressions which correspond by position to the **<argument ports>** of the definition. Port arguments in the definition may be **input**, **inout** or **output**. Since the **<argument ports>** in the task definition look like declarations, the programmer must be careful in adding declares at the beginning of a task.

# Tasks and Functions

```
// Testing tasks and functions
```

```
module tasks;
```

```
task add;    // task definition
```

```
input a, b;  // two input argument ports
```

```
output c;    // one output argument port
```

```
reg R;       // register declaration
```

```
begin
```

```
    R = 1;
```

```
    if (a == b)
```

```
        c = 1 & R;
```

```
    else
```

```
        c = 0;
```

```
end
```

```
endtask
```

# Tasks and Functions

Task Continue...

```
initial begin: init1
```

```
    reg p;
```

```
    add(1, 0, p); // invocation of task with 3 arguments
```

```
    $display("p= %b", p);
```

```
end
```

```
endmodule
```

# Tasks and Functions

**input** and **inout** parameters are passed by value to the task and **inout** parameters are passed back to invocation by value of **output**.  
**Call by reference** is not available.

- Allocation of all variables is static
- A task may call itself but each invocation of the task uses the same storage
- Since concurrent threads may invoke the same task, the programmer must be aware of the static nature of storage and avoid unwanted overwriting of shared storage space.

# Tasks and Functions

- The purpose of a function is to return a value that is to be used in an expression
- A function definition must contain at least one **input** argument
- The definition of the function is as below:

```
function <range or type> <function name>;// Notice: no parameter list or ()s  
<argument ports>  
<declarations>  
<statements>  
endfunction
```

# Tasks and Functions

```
// Testing functions
```

```
module functions;
```

```
function [1:1] add2; // function definition
```

```
input a, b; // two input argument ports
```

```
reg R; // register declaration
```

```
begin R = 1;
```

```
if (a == b) add2 = 1 & R;
```

```
else add2 = 0;
```

```
end
```

```
endfunction
```



initial

begin: init1 reg p; p = add2(1, 0); // invocation of function with  
2 arguments

\$display("p= %b", p);

end

endmodule



# Register Inference

- Allow sequential logic design
- Keep technology independent
- Latch — a level-sensitive memory device
- Flip-Flop — an edge-triggered memory device
  
# Flip-Flop Inference

- Wire (port) assigned in the synchronous section

```
module FF_PN (Clock, X1, X2, Y1, Y2);  
  input Clock;  
  input X1, X2;  
  output Y1, Y2;  
  
  reg Y1, Y2;  
  
  always @(posedge Clock)  
    Y1 = X1;  
  
  always @(negedge Clock)  
    Y2 = X2;  
  
endmodule
```



# Flip-Flop Inference

- Asynchronous / synchronous reset / enable

```
module FFS (Clock, SReset, ASReset, En, Data1, Data2, Y1, Y2
  Y3, Y4, Y5, Y6);
  input Clock, SReset, ASReset, En, Data1, Data2;
  output Y1, Y2, Y3, Y4, Y5, Y6;
  reg Y1, Y2, Y3, Y4, Y5, Y6;

  always @(posedge Clock)
  begin
    // Synchronous reset
    if (! SReset)
      Y1 = 0;
    else
      Y1 = Data1 | Data2;
  end
end
```

# Flip-Flop Inference

```
// Negative active asynchronous reset
always @(posedge Clock or negedge ASReset)
  if (! ASReset)
    Y2 = 0;
  else
    Y2 = Data1 & Data2;
```

```
// One synchronous & one asynchronous reset
always @(posedge Clock or negedge ASReset)
  if(! ASReset)
    Y3 = 0;
  else if (SReset)
    Y3 = 0;
  else
    Y3 = Data1 | Data2;
```

# Flip-Flop Inference

```
// Single enable
always @(posedge Clock)
  if (En)
    Y4 = Data1 & Data2;

// Synchronous reset and enable
always @(posedge Clock)
  if (SReset)
    Y5 = 0;
  else if (En)
    Y5 = Data1 | Data2;

endmodule
```

# Latch Inference

- Incompletely specified wire (port) in the synchronous section

- D latch

always @(enable or data)

if (enable)


q = data;

- D latch with gated asynchronous data

always @(enable or data or gate)

if (enable)

q = data & gate;

 


# More Latches

- D latch with gated “enable”

always @(enable or d or gate)

if (enable & gate)

q = d;

 

- D latch with asynchronous reset

always @(reset or data or gate)

if (reset)

q = 1'b0;

else if (enable)

q = data;



# Avoid Latch Inference

- Avoiding latch inference

```
always @(PHI_1 or A) begin
    Y = 0;
    if (PHI_1)
        Y = A;
end
```


- Another way

```
always @(PHI_1 or A) begin
    if (PHI_1)
        Y = A;
    else
        Y = 0;
end
```
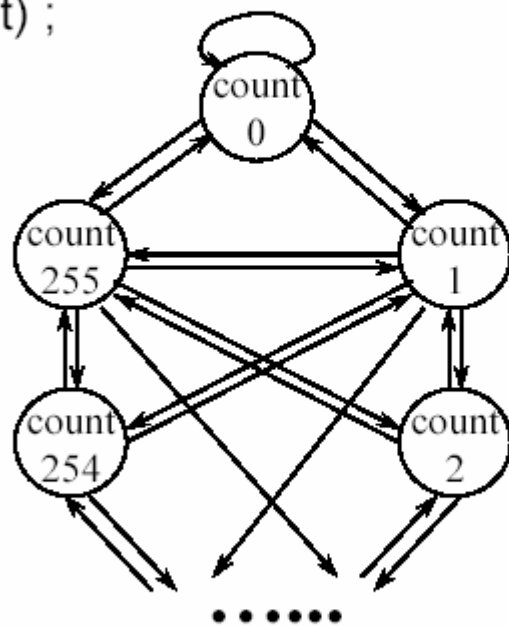
# 1-Process FSM

- Lump all descriptions into a single process

```
module counter (clk, rst, load, in, count) ;  
input      clk, rst, load ;  
input  [7:0] in ;  
output [7:0] count ;  
reg    [7:0] count ;  
  
always @(posedge clk) begin  
    if (rst) count = 0 ;  
    else if (load) count = in ;  
    else if (count == 255) count = 0 ;  
    else count = count + 1 ;  
end  
endmodule
```



256 states 66047 transitions

# Verilog Template [1]

```
module <module_name> (<ports>)  
  
input <input_port_names>;  
  
output <output_port_names>;  
  
reg <outputs_and_values_to_be_used_in_always_blocks>;  
  
wire <values_to_be_used_in_continuous_assignments>;  
  
//wire outputs do not need to be declared again  
  
<called_module_name> U1(<module_ports>);  
  
<called_module_name> U2(<module_ports>);  
  
....
```

# Verilog Template [2]

//continuous assignment

**assign** *<wire\_name>* = *<operation\_of\_wire\_and\_reg>*;

//combinational always -> use blocking assignment “=”

**always@** (*<wire\_or\_reg1>* **or** *<wire\_or\_reg2>* ..) **begin**

*<combinational\_reg\_name>* = *<operation\_of\_wire\_and\_reg>*;

**end**

# Verilog Template [3]

//sequential always -> use non-blocking assignment “<=“

**always@** (posedge clk **or** negedge reset) **begin**

**if**(!reset) **begin**

    <*sequential\_reg\_names*> <= 0; //reset reg values

**end**

**else begin**

    <*sequential\_reg\_names*> <= <*operation\_of\_wire\_and\_reg*>;

**end**

**endmodule**

# Outline

- Introduction
- Language elements
- Gate-level modeling
- Data-flow modeling
- Behavioral modeling
- Modeling examples
- Simulation and test bench

# Simulation

- Design, stimulus, control, saving responses, and verification can be completed in a single language
  - Stimulus and control
    - Use initial procedural block
  - Saving responses
    - Save on change
    - Display data
  - Verification
    - Automatic compares with expected responses
- The behavior of a design can be simulated by HDL simulators
  - Test benches are given by users as the inputs of the design
  - Some popular simulators
    - Verilog-XL (Cadence™, direct-translate simulator)
    - NC-Verilog (Cadence™, compiled-code simulator)
    - VCS (ViewLogic™, compiled-code simulator)

# Supports for Verification

- Text output (show results at standard output)
  - **\$display**: print out the current values of selected signals
    - Similar to the `printf()` function in C language
  - **\$write**: similar to **\$display** but it does not print a “\n”
  - **\$monitor**: display the values of the signals in the argument list whenever any signal changes its value
  - Examples:

```
$display (“A=%d at time %t”, A, $time);
```

```
A=5 at time 10
```

```
$monitor (“A=%d CLK=%b at time %t”, A, CLK, $time);
```

```
A=2 CLK=0 at time 0
```

```
A=3 CLK=1 at time 5
```

```
.....
```



# Test Bench

```
module test_bench;  
  data type declaration  
  module instantiation  
  applying stimulus  
  display results  
endmodule
```

- A test bench is a top level module without inputs and outputs
- Data type declaration
  - Declare storage elements to store the test patterns
- Module instantiation
  - Instantiate pre-defined modules in current scope
  - Connect their I/O ports to other devices
- Applying stimulus
  - Describe stimulus by behavior modeling
- Display results
  - By text output, graphic output, or waveform display tools

# Example Testfixture

```
`timescale 1ns / 1ps
```

```
reg [7:0] id1[0:63999];
```

```
reg [7:0] id2[0:63999];
```

```
reg [7:0] a[0:8];
```

```
integer c;
```

```
initial
```

```
begin
```

```
$readmemh ("e:\\matlabr12\\work\\clowngray.txt",id1);
```

```
$readmemh ("e:\\matlabr12\\work\\cartmangray.txt",id2);
```

```
a[0]=100;
```

```
a[1]=125;
```

```
a[2]=100;
```

```
a[3]=125;
```

```
a[4]=200;
```

```
a[5]=125;
```

```
a[6]=100;  
a[7]=125;  
a[8]=100;
```

```
#5 RST=1'b0;  
#1 RST=1'b1;  
#2 ModSel=1'b0;  
#1431 StartFrame=1'b1;  
InSelect=1'b0;  
#1000 StartFrame=0;
```

```
$writememh("e:\\matlabr12\\work\\filtered1.txt",id3,0,63999);  
$writememh("e:\\matlabr12\\work\\filtered2.txt",id4,0,63999);
```

```
#100 $finish;
```

```
end
```

```
always@ #50 CLK=~CLK;
```

```
always@(posedge RAMclk)
```

```
begin
```

```
    if(OutWrite==0)
```

```
        begin
```

```
            if (OutSelect==1'b0)
```

```
                id3[AddOut16[15:0]]=DOut8[7:0];
```

```
            else
```

```
                id4[AddOut16[15:0]]=DOut8[7:0];
```

```
        end
```

```
end
```

Some useful Verilog links,

<http://www.cs.du.edu/~cag/courses/ENGR/ence3830/VHDL/>

<http://www.see.ed.ac.uk/~gerard/Teach/Verilog/manual/>

<http://oldeee.see.ed.ac.uk/~gerard/Teach/Verilog/manual/>

[http://www.ece.utexas.edu/~patt/02s.382N/tutorial/verilog\\_manu](http://www.ece.utexas.edu/~patt/02s.382N/tutorial/verilog_manu)

<http://www.eg.bucknell.edu/~cs320/1995-fall/verilog-manual.htm>

<http://mufasa.informatik.uni-mannheim.de/lisra/persons/lars/verilo>

[http://www.sutherland-hdl.com/on-line\\_ref\\_guide/vlog\\_ref\\_top.ht](http://www.sutherland-hdl.com/on-line_ref_guide/vlog_ref_top.ht)

<http://www-cad.eecs.berkeley.edu/~chinnery/synthesizableVerilo>

<http://ee.ucd.ie/~finbarr/verilog/>

<http://athena.ee.nctu.edu.tw/courses/CAD/>