

Software Engineering 2DA4

Slides 9: Asynchronous Sequential Circuits

Dr. Ryan Leduc

Department of Computing and Software
McMaster University


Material based on S. Brown and Z. Vranesic, *Fundamentals of Digital Logic with Verilog Design, 3rd Ed.*

Asynchronous Inputs

- ▶ Synchronous sequential circuits use flip-flops to store the current state.
- ▶ State changes occur on the positive or negative clock edge.
- ▶ For **synchronous inputs**, changes occur shortly after the active clock edge since inputs of one circuit are typically outputs of another synchronous circuit driven by same clock.
- ▶ **Asynchronous inputs** may change at any time. e.g. pushbutton inputs, outputs from a circuit driven by a different clock.
- ▶ Problems:
 - a) Propagation delays can cause signals to be interpreted as different values in different parts of the circuit.
 - b) Asynchronous inputs may violate the setup and hold times of flip flops.

Synchronizing Inputs

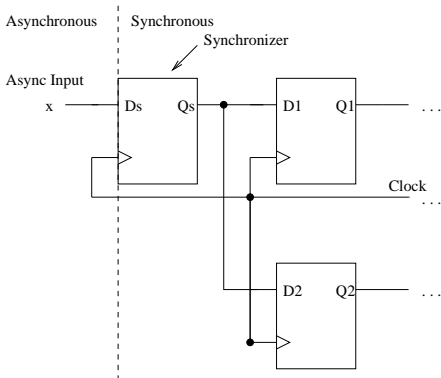- ▶ Always put asynchronous inputs into a **synchronizer**.
- ▶ If the asynchronous input x was connected directly to D1 and D2, propagation delays could cause Q1 and Q2 to latch different values.



Metastability


- ▶ **Q:** What happens when flip-flop setup and hold times are violated for synchronizer?
- ▶ **A:** Flip-flop may enter **metastable state** where logic value is neither 1 nor 0. Flip-flop will eventually resettle to either 1 or 0 after an indeterminate amount of time.
- ▶ If such a *synchronizer failure* occurs, the only guaranteed way to recover is to reset the entire circuit!
- ▶ While probability of synchronizer failure is usually small, it can never be eliminated. Good design though can reduce the probability of such failures.

Reducing Metastability Problems

- ▶ Synchronizer failure can be reduced by the following methods:
 - ▶ Using faster flip-flops with smaller setup and hold times (reduces size of vulnerable time window).
 - ▶ Lengthening the system clock period or, if possible, sampling the input at a lower frequency (reduces number of vulnerable time windows).


Reducing Metastability Problems - II

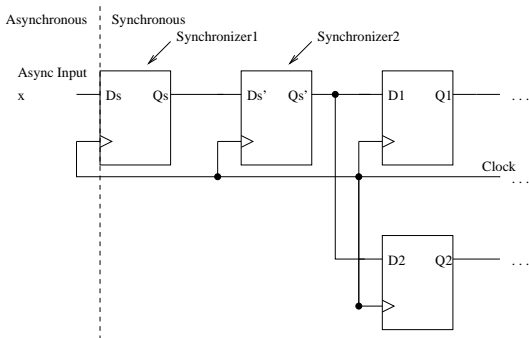- ▶ Another common method uses a 2-bit shift register as synchronizer.
- ▶ If 1st synchronizer flip-flop enters metastable state, it will usually settle to a proper logic value before next active clock edge.
- ▶ This introduces a delay of one clock period on input.



Asynchronous vs. Synchronous Sequential Circuits

 - ▶ For the general model of a sequential circuit, inputs and current state are used by combinational circuits to compute outputs and next state.
- ▶ After a time delay (say Δ) the next state becomes the current state.
 - ▶ For synchronous circuits, $\Delta =$ clock period
 - ▶ For asynchronous circuits, $\Delta =$ total propagation delay



Asynch vs. Synch Sequential Circuits - II

- ▶ Asynchronous circuits change when inputs change while synchronous circuits change on clock edge.
- ▶ Synchronous circuits assume that inputs do not change too close to active clock edge.
- ▶ Main assumptions for Asynchronous circuits:
 1. Only 1 input changes at a time
 2. Input changes occur sufficiently far apart to allow the circuit to reach a stable state before the next change.
- ▶ A **stable state** is a state the asynchronous circuits will stay in once reached, until another input changes.

Asynch vs. Synch Sequential Circuits - III

- ▶ Asynchronous advantages:
 - ▶ **Speed:** no clock involved; speed only depends upon propagation delays.
 - ▶ **Flexibility:** different parts of an asynchronous system can operate at different speeds (each limited by their propagation delay) while in synchronous systems, clock frequency has to accommodate slowest part.
 - ▶ **Power usage:** distributing clock signal to all parts of an synchronous system adds to power usage, up to 30-40% for a high performance circuit.
- ▶ Asynchronous disadvantages:
 - ▶ **Design complexity:** difficult to design, and limited tool support.
 - ▶ **Glitches:** race conditions, “glitches” can cause problems if circuits not carefully designed.

Asynchronous Terminology

- ▶ For asynchronous circuits we use the following terminology:


Flow Table: refers to state table.

Excitation Table: refers to state-assigned table.

- ▶ A state in a flow table is *stable* for particular set of inputs when the Next state = Current state.
- ▶ Otherwise the state is **unstable** and will change. We denote stable states in a flow table by circling them (e.g. (A)).

SR-latch as Asynchronous Sequential Circuit

- ▶ To obtain state variables, we use the natural gate delay of circuit.
- ▶ We cut the feedback loop and insert a delay element.
- ▶ Creates a delay of time Δ , equal to the combined propagation delay of the two NOR gates.
- ▶ We then treat the NOR gates as ideal gates with zero delay.
- ▶ We take y (output of delay element) to be the present state, and Y to be our next state variable (input to delay element).
- ▶ After time delay Δ , y is assigned the value of Y .

 

(b) Circuit with modeled gate delay

SR-latch as Asynch Sequential Circuit - II

- ▶ We take Q to be our output variable, where $Q = y$.
- ▶ We now derive an equation for Y in terms of S , R , and y .
- ▶ Taking point A as output of leftmost NOR gate, we have:

$$A = \overline{(S + y)}$$

- ▶ Thus: $Y = \overline{R + \overline{(S + y)}} = \overline{R} \cdot (S + y)$
- ▶ Using this equation, we can construct the excitation table below.

Present state	Next state			
	SR = 00	01	10	11
y	Y	Y	Y	Y
0	0	0	1	0
1	1	0	1	0


(b) Excitation table

SR-latch as Asynch Sequential Circuit - III

- ▶ If we take $y = 0$ to be state A, and $y = 1$ to be state B, we can convert the excitation table to the flow diagram below.
- ▶ From the flow table, we can easily derive the state diagram below.
- ▶ Note that asynchronous circuits have no RESET state.
- ▶ Their initial state is random.

Present state	Next state				Output
	SR = 00	01	10	11	
A	\textcircled{A}	\textcircled{A}	B	\textcircled{A}	0
B	\textcircled{B}	A	\textcircled{B}	A	1

(a) Flow

 


(b) State diagram

Analysis of Asynchronous Sequential Circuits

- ▶ An asynchronous sequential circuit can be analyzed by the following steps:
 1. Cut each feedback path and insert a delay.
 2. Determine Next State and Output expressions from circuit.
 3. Derive excitation table (async state assignment table) from Next State and Output equations.
 4. Obtain a flow table (async state table) by assigning state labels to each of the state encodings.
 5. Draw FSM from flow table.

Analysis of Gated D Latch

 - Derive equations for output Q and next state Y for gated D latch and use to derive excitation, flow and state diagram.




(a) Circuit

Present state y	Next state				
	$CD = 00$	01	10	11	
0	0	0	0	1	0
1	1	1	0	1	1

(b) Excitation table

Present state	Next state				Q
	$CD = 00$	01	10	11	
A	(A)	(A)	(A)	B	0
B	(B)	(B)	A	(B)	1


(c) Flow table

 

 (d) State diagram

Analysis of Master-Slave D Flip-flop

- ▶ Derive equations for output Q and next state variables Y_m and Y_s for master-slave D flip-flop, and use them to derive excitation, flow and state diagram.
- ▶ We will use y_m and y_s as our current state variables, and use the next state equations from gated D latch as our starting point (see discussion in class).
- ▶ NOTE: input C is the clock in a synchronous setting, but here it is just another input.



Analysis of Master-Slave D Flip-flop - II

- Using derived equations, we can fill in the tables below.

Present state $y_m y_s$	Nextstate				Output Q
	$CD = 00$	01	10	11	
00	$\overline{(00)}$	$\overline{(00)}$	$\overline{(00)}$	10	0
01	00	00	$\overline{(01)}$	11	1
10	11	11	00	$\overline{(10)}$	0
11	$\overline{(11)}$	$\overline{(11)}$	01	$\overline{(11)}$	1


(a) Excitationtable

Present state	Nextstate				Output Q
	$CD = 00$	01	10	11	
S1	$\overline{(S1)}$	$\overline{(S1)}$	$\overline{(S1)}$	S3	0
S2	S1	S1	$\overline{(S2)}$	S4	1
S3	S4	S4	S1	$\overline{(S3)}$	0
S4	$\overline{(S4)}$	$\overline{(S4)}$	S2	$\overline{(S4)}$	1

 (b) Flowtable

Analysis of Master-Slave D Flip-flop - III

- ▶ Using flow table, we can construct state diagram below.
- ▶ Read example 9.3 in text on own.



Unspecified Entries

- ▶ For synthesis, can simplify by adding unspecified states when a particular input combination can't occur at a given state.
- ▶ Consider present state S2, and input combination $CD = 01$.
- ▶ This combination will never occur in normal operation, as S2 is only stable for $CD = 10$ and $CD = 01$ requires two input changes, both of which are not stable.
- ▶ For i.e., if we have path $CD = 10$ to $CD = 00$, this would take us to state S1, before we got change $CD = 01$ both stable for S1.

Present state	Next state				Output Q
	$CD = 00$	01	10	11	
S1	(S1)	(S1)	(S1)	S3	0
S2	S1	S1	(S2)	S4	1
S3	S4	S4	S1	(S3)	0
S4	(S4)	(S4)	S2	(S4)	1

(b) Flowtable

Present state	Next state				Output Q
	$CD = 00$	01	10	11	
S1	(S1)	(S1)	(S1)	S3	0
S2	S1	-	(S2)	S4	1
S3	-	S4	S1	(S3)	0
S4	(S4)	(S4)	S2	(S4)	1

(c) Flow Table with unspecified entries

Synthesis of Asynchronous Sequential Circuits

1. Derive state diagram.
2. Derive flow table (reduce states: we won't cover this).
3. Perform state assignments and derive excitation table.

Ensure state variables do not contain *race conditions*.

4. Obtain next state and output expressions and ensure that they do not contain hazards (Section 9.6).
5. Construct circuit that implements these expressions.

Asynchronous Design Example: Serial Parity Generator

- ▶ **Problem:** Design an asynchronous sequential circuit that implements a FSM that acts as an even serial parity generator.
- ▶ Circuit receives series of pulses on input w .
- ▶ When odd number of pulses have been received, output z is 1.
- ▶ When even number of pulses received, output z is 0.
- ▶ NOTE: in an asynchronous circuit, we have no timing information.
- ▶ To detect a pulse, we need to detect when input goes from 0 to 1 (start of pulse), and then when it goes from 1 to 0 (end of pulse).
- ▶ See design of state diagram in class on board.

Serial Parity Generator: tables

- ▶ From state diagram on board, we can write out flow diagram below.
- ▶ We will see on next slide why first state assignment is bad.

Present State	Next state		Output z
	$w = 0$	$w = 1$	
A	(A)	B	0
B	C	(B)	1
C	(C)	D	1
D	A	(D)	0

(b) Flow table

Present state y_2y_1	Next state		Output z
	$w = 0$	$w = 1$	
	$Y_2 Y_1$		
00	(00)	01	0
01	10	(01)	1
10	(10)	11	1
11	00	(11)	0

(a) Poor state assignment

Present state y_2y_1	Next state		Output z
	$w = 0$	$w = 1$	
	$Y_2 Y_1$		
00	(00)	01	0
01	11	(01)	1
11	(11)	10	1
10	00	(10)	0

(b) Good state assignment

State Assignments for Asynchronous FSMs

- ▶ Figure below contains two different possible state assignments for serial parity FSM.
- ▶ **Problem:** table (a) requires transition

$$y_2y_1 = 11 \xrightarrow{w=0} y_2y_1 = 00$$

- ▶ This requires y_1 and y_2 to change at exactly the same time!
- ▶ Since the circuit is not ideal, y_1 and y_2 will not change at the same time.

Present state y_2y_1	Next state		Output z
	$w = 0$	$w = 1$	
	Y_2Y_1		
00	(00)	01	0
01	10	(01)	1
10	(10)	11	1
11	00	(11)	0

(a) Poor state assignment

Present state y_2y_1	Next state		Output z
	$w = 0$	$w = 1$	
	Y_2Y_1		
00	(00)	01	0
01	11	(01)	1
11	(11)	10	1
10	00	(10)	0

(b) Good state assignment

State Assignments for Asynchronous FSMs - II

- ▶ **Case 1:** y_1 changes 1st. Circuit changes to $y_2y_1 = 10$ corresponding to state C and then stays in C producing wrong output.
- ▶ **Case 2:** y_2 changes first. Circuit changes to $y_2y_1 = 01 =$ state B . Then tries to change to state $C = 10$. This requires $01 \rightarrow 10$, another simultaneous change. This means that y_2 must change again.
- ▶ Since we are assuming y_2 changed first, y_1 should complete its change to 0 first (before y_2 can change again), bringing the state to 00.

Present state y_2y_1	Next state		Output z
	$w = 0$	$w = 1$	
	Y_2Y_1		
00	00	01	0
01	10	01	1
10	10	11	1
11	00	11	0

(a) Poor state assignment

Present state y_2y_1	Next state		Output z
	$w = 0$	$w = 1$	
	Y_2Y_1		
00	00	01	0
01	11	01	1
11	11	10	1
10	00	10	0

(b) Good state assignment

State Assignments for Asynchronous FSMs - III

- ▶ As state $00 = A$ is correct and stable for $w = 0$, we arrive at the correct answer.
- ▶ The correct outcome depends on which variable changes first. This is referred to as a **race condition**.

Present state y_2y_1	Next state		Output z
	$w = 0$	$w = 1$	
	Y_2Y_1		
00	(00)	01	0
01	10	(01)	1
10	(10)	11	1
11	00	(11)	0

(a) Poor state assignment

Present state y_2y_1	Next state		Output z
	$w = 0$	$w = 1$	
	Y_2Y_1		
00	(00)	01	0
01	11	(01)	1
11	(11)	10	1
10	00	(10)	0

(b) Good state assignment

Eliminating Race Conditions

- ▶ Treat state variables like inputs to circuit:
- ▶ Only allow one variable to change at a time (grey code!).

Want state change pattern: A B C D
00 --> 01 --> 11 --> 10
 ^ |

- ▶ Table (b) uses this state assignment.

Present state $y_2 y_1$	Next state		Output z
	$w = 0$	$w = 1$	
00	00	01	0
01	10	01	1
10	10	11	1
11	00	11	0

(a) Poor state assignment

Present state $y_2 y_1$	Next state		Output z
	$w = 0$	$w = 1$	
00	00	01	0
01	11	01	1
11	11	10	1
10	00	10	0

(b) Good state assignment



Implementing FSM

- ▶ From excitation table (b), we can derive our output and next state equations.
- ▶ For our output, we have: $z = y_1$.
- ▶ For our next state equations we have:

$$Y_1 = w\bar{y}_2 + \bar{w}y_1 + y_1\bar{y}_2$$
$$Y_2 = \underbrace{wy_2 + \bar{w}y_1}_{k\text{-maps}} + \underbrace{y_1y_2}_{\text{stop hazards}}$$

Implementing FSM - II

  - ▶ Below is circuit for FSM.
- ▶ On the right is the synchronous equivalent.



Hazards

- ▶ In an asynchronous sequential circuit, want to avoid *glitches* on signals.
- ▶ A glitch is when a signal temporary takes on the wrong value:

-----|⁻|----- should always be zero.

- ▶ Glitches caused by structure of circuit and propagation delays are called **hazards**.

Types of Hazards

- ▶ There are two types:

Static Hazards: When signal is not suppose to change its value in response to a specific change in an input, but instead momentarily does change.

Dynamic Hazards: This is when a signal is suppose to change value, but there is a small oscillation.



(a) Static hazard




(b) Dynamic hazard

Static Hazards


- ▶ A change to a primary input often has more than one path of propagation to an output.
- ▶ When one path has a longer propagation delay than the others, we may find a static hazard.
- ▶ This can be eliminated by examining the k-map of the output.
- ▶ A potential hazard exists whenever two adjacent ones (or 0's if we are doing a product-of-sum implementation) are not covered by a common product term (sum term for product-of-sum).
- ▶ To guarantee no static hazards, obtain a cover such that each pair of adjacent one's (zero's) is covered by a common product term (sum term).

Static Hazard Example

 
- ▶ Top circuit is the minimal k-map version and it contains a static hazard as shown on next slide.
- ▶ Minimal circuit (black groupings) have two adjacent 1 terms (x_1x_2 goes from 01 to 11), thus could have static hazard.
- ▶ In k-map, the blue grouping is added to ensure no hazards.
- ▶ Bottom circuit contains all three terms, thus no static hazards.



(a) Circuit with a hazard

 


(b) Karnaugh map

 

 (c) Hazard-free circuit

Static Hazard Example - II


- ▶ Using a k-map, we can see if a circuit might have static hazards, and how to ensure they don't.
 - ▶ The kmap also indicates where to look for a static hazard (input combinations that go between two adjacent one terms that are not covered by a common product term.)
-
- ▶ For the hazard to exist, we need two paths with different propagation delays.
 - ▶ We can use a timing diagram to show the existence of a hazard as below.



Checking State Variables for Static Hazards


- ▶ This means checking the next state variables (ie. Y_1 , not y_1).
 - ▶ Ignore output logic.
 - ▶ Ignore feedback path. Treat present state variables as “just another input” to your circuit.
 - ▶ Derive equations for each next state variable and write down its k-map.
 - ▶ Analyze each k-map for potential static hazards.

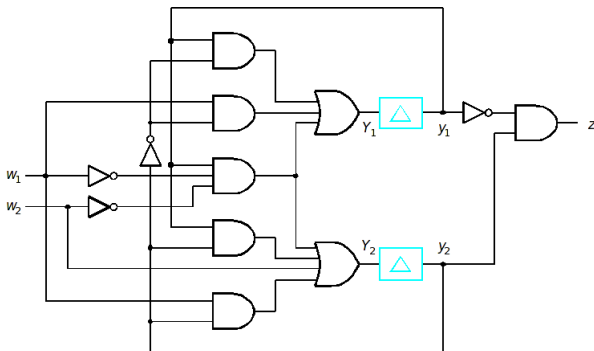Checking State Variables for Static Hazards - II




Dynamic Hazards

- ▶ Figure shows an example of a dynamic hazard.
- ▶ A dynamic hazard is caused by the structure of a circuit.
- ▶ It's caused by a circuit with more than two levels, in which changes to an input have more than one path to propagate along.
- ▶ In Figure, there are three paths.
- ▶ A circuit with a dynamic hazard must also contain a static hazard. The figure has a static hazard at point b.
- ▶ To avoid dynamic hazards, design two-level circuits with no static hazards.

 

(a) Circuit

 

(b) Timing diagram