

Symbolic Evaluation of Hadamard-Toffoli Quantum Circuits

Jacques Carette, Amr Sabry, Gerardo Ortiz

January 16, 2023

Introduction

Idea

Reversible

Superposition

Symbolic

Big Picture

Retrodictive

Examples

Software

Requirements

Design

Evaluation

Running

Timings

Complexity


Conclusion

Extras

Cost Models

Traditional partial evaluation and symbolic evaluation techniques apply to an interesting class of quantum circuits with surprising effectiveness!

Reversible gates

 

$$CX(0, b) = (0, b)$$

$$CX(1, b) = (1, \bar{b})$$

So, writing inputs/outputs horizontally:

$$|0111\rangle \Rightarrow |0111\rangle$$

$$\Rightarrow |0111\rangle$$

$$\Rightarrow |0101\rangle$$

$$\Rightarrow |0100\rangle$$

$$|1100\rangle \Rightarrow |1110\rangle$$

$$\Rightarrow |1111\rangle$$

$$\Rightarrow |1101\rangle$$

$$\Rightarrow |1100\rangle$$

$$|1010\rangle \Rightarrow |1000\rangle$$

$$\Rightarrow |1001\rangle$$

$$\Rightarrow |1001\rangle$$

$$\Rightarrow |1001\rangle$$


$$|1111\rangle \Rightarrow |1101\rangle$$

$$\Rightarrow |1100\rangle$$

$$\Rightarrow |1110\rangle$$

$$\Rightarrow |1111\rangle$$

Superpositions

 

$$H|0\rangle = \frac{1}{\sqrt{2}}|0\rangle + \frac{1}{\sqrt{2}}|1\rangle = \frac{1}{\sqrt{2}}(|0\rangle + |1\rangle)$$

So the top two wires are in the state

$$\frac{1}{\sqrt{2}}(|0\rangle + |1\rangle) \otimes \frac{1}{\sqrt{2}}(|0\rangle + |1\rangle) = \frac{1}{2}(|00\rangle + |10\rangle + |01\rangle + |11\rangle)$$

Introduction

Idea

Reversible

Superposition

Symbolic

Big Picture

Retrodictive

Examples

Software

Requirements

Design

Evaluation

Running

Timings


Complexity

Conclusion

Extras

Cost Models

Superpositions

 


$$H|0\rangle = \frac{1}{\sqrt{2}}|0\rangle + \frac{1}{\sqrt{2}}|1\rangle = \frac{1}{\sqrt{2}}(|0\rangle + |1\rangle)$$

Thus for the whole circuit:

$$\begin{aligned} |0000\rangle &\Rightarrow \frac{1}{2}(|0000\rangle + |0100\rangle + |1000\rangle + |1100\rangle) \\ &\Rightarrow \frac{1}{2}(|0000\rangle + |0100\rangle + |1010\rangle + |1110\rangle) \\ &\Rightarrow \frac{1}{2}(|0000\rangle + |0100\rangle + |1011\rangle + |1111\rangle) \\ &\Rightarrow \frac{1}{2}(|0000\rangle + |0110\rangle + |1011\rangle + |1101\rangle) \\ &\Rightarrow \frac{1}{2}(|0000\rangle + |0111\rangle + |1011\rangle + |1100\rangle) \end{aligned}$$

Symbolic Execution (new)

Replace $\frac{1}{\sqrt{2}}(|0\rangle + |1\rangle)$ by a symbolic variable:

 

Maintain formula in algebraic normal form (ANF).

So

$$\begin{aligned}
 |xy00\rangle &\Rightarrow |xyx0\rangle \\
 &\Rightarrow |xyxx\rangle \\
 &\Rightarrow |xy(x \oplus y)x\rangle \\
 &\Rightarrow |xy(x \oplus y)(x \oplus y)\rangle
 \end{aligned}$$

Quantum Circuits

Introduction

Idea
Reversible
Superposition
Symbolic

Big Picture

Retrodictive

Examples

Software

Requirements
Design


Evaluation

Running
Timings
Complexity

Conclusion

Extras

Cost Models

 

- U_f is a *classical reversible* circuit representing f , i.e. $U_f(\mathbf{x}, \mathbf{y}) = |\mathbf{x} \ (\mathbf{y} \oplus \mathbf{f}(\mathbf{x}))\rangle$.
- H is the Hadamard gate; introduces *quantum parallelism* to evaluate U_f for many inputs simultaneously.
- QFT is the Quantum Fourier Transform used to analyze the spectral properties of the output.

Quantum Circuits

Introduction

Idea
Reversible
Superposition
Symbolic

Big Picture

Retrodictive

Examples

Software

Requirements
Design


Evaluation

Running
Timings
Complexity

Conclusion

Extras

Cost Models

 

- U_f is a *classical reversible* circuit representing f , i.e. $U_f(\mathbf{x}, \mathbf{y}) = |\mathbf{x} \ (\mathbf{y} \oplus \mathbf{f}(\mathbf{x}))\rangle$.
- H is the Hadamard gate; introduces *quantum parallelism* to evaluate U_f for many inputs simultaneously.
- QFT is the Quantum Fourier Transform used to analyze the spectral properties of the output.

Quantum Circuits Retrodictive Evaluation

Introduction

Idea
Reversible
Superposition
Symbolic

Big Picture

Retrodictive

Examples

Software

Requirements
Design


Evaluation

Running
Timings
Complexity

Conclusion

Extras

Cost Models

 

- U_f is a *classical reversible* circuit representing f , i.e. $U_f(\mathbf{x}, \mathbf{y}) = |\mathbf{x} \ (\mathbf{y} \oplus \mathbf{f}(\mathbf{x}))\rangle$.
- H is the Hadamard gate; introduces *quantum parallelism* to evaluate U_f for many inputs simultaneously.
- QFT is the Quantum Fourier Transform used to analyze the spectral properties of the output.

Introduction

Idea
Reversible
Superposition
Symbolic

Big Picture

Retrodictive

Examples

Software

Requirements
Design

Evaluation

Running
Timings
Complexity

Conclusion

Extras

Cost Models

- 1 Deutsch
- 2 Deutsch-Jozsa
- 3 Bernstein-Varizani
- 4 Simon
- 5 Grover
- 6 Shor

Examples

Introduction

Idea
Reversible
Superposition
Symbolic

Big Picture

Retrodictive

Examples

Software

Requirements
Design

Evaluation

Running
Timings
Complexity

Conclusion

Extras

Cost Models

- 1 Deutsch
- 2 Deutsch-Jozsa
- 3 Bernstein-Varizani
- 4 Simon
- 5 Grover
- 6 Shor

Examples: Deutsch and Deutsch-Josza

Introduction

Idea
Reversible
Superposition
Symbolic

Big Picture

Retrodictive

Examples

Software

Requirements
Design

Evaluation

Running
Timings
Complexity

Conclusion

Extras

Cost Models

Definition

A boolean function is **balanced** if it outputs the same number of 0/1 outputs.

Deutsch:

Problem

Given $f : \mathbb{B} \rightarrow \mathbb{B}$, decide if f is constant or balanced.

Deutsch-Josza:

Problem

Given $f : \mathbb{B}^n \rightarrow \mathbb{B}$, where f is known to be constant or balanced, decide which one it is.

Examples: Grover and Shor

Introduction

Idea
Reversible
Superposition
Symbolic

Big Picture

Retrodictive

Examples

Software

Requirements
Design

Evaluation

Running
Timings
Complexity

Conclusion

Extras

Cost Models

Grover:

Problem

Given $f : \mathbb{B}^n \rightarrow \mathbb{B}$ where there exists a unique u such that $f(u) = 1$. Find u .

Shor:

Problem

Factor a given N . Do this by using $f(x) = a^x \bmod N$ for suitable a and $f : \mathbb{B}^Q \rightarrow \mathbb{B}^n$ with $Q = \lceil \log_2(N^2) \rceil$, $n = \lceil \log_2 N \rceil$.

Requirements

Variabilities:

- ① **multiple representations** of boolean **values**,
- ② **multiple representations** of boolean **formulae**,
- ③ **different evaluation** means (directly, symbolically, forwards, backwards, retrodictive).

Possible to implement:

- ④ a **reusable representation** of our circuits,
- ⑤ a **reusable representation** of the inputs, outputs and ancillae,
- ⑥ a **synthesis algorithm** for $\mathbb{B}^n \rightarrow \mathbb{B}$ functions
- ⑦ a **reusable library** of circuits

Also, non-functional characteristics to hold:

- ⑧ evaluation of **reasonably-sized circuits** should be **reasonably efficient**.

Design

Introduction

Idea
Reversible
Superposition
Symbolic

Big Picture

Retrodictive

Examples

Software

Requirements

Design

Evaluation

Running
Timings
Complexity

Conclusion

Extras

Cost Models

```
class (Show v, Enum v) => Value v where
```

```
  zero :: v
```

```
  one  :: v
```

```
  snot :: v -> v
```

```
  sand :: v -> v -> v
```

```
  sxor :: v -> v -> v
```

```
-- has a default implementation
```

```
snand :: [v] -> v -- n-ary and
```

```
snand = foldr sand one
```

Implemented **four** times.

Introduction

Idea
Reversible
Superposition
Symbolic

Big Picture

Retroductive

Examples

Software

Requirements

Design

Evaluation

Running
Timings
Complexity

Conclusion

Extras

Cost Models

```
class (Show v, Enum v) => Value v where
```

```
  zero :: v
```

```
  one  :: v
```

```
  snot :: v -> v
```

```
  sand :: v -> v -> v
```

```
  sxor :: v -> v -> v
```

```
  -- has a default implementation
```

```
  snand :: [v] -> v -- n-ary and
```

```
  snand = foldr sand one
```

Implemented **four** times.

```
data VarInFormula f v = FR
```

```
  { fromVar  :: v -> f
```

```
  , fromVars :: Int -> v -> [ f ]
```

```
  }
```


Design

First, naïve implementation:

```
newtype Ands = Ands { lits :: [String] }
  deriving (Eq, Ord)
```

```
(&&&) :: Ands -> Ands -> Ands
(Ands lits1) &&& (Ands lits2) =
  Ands (lits1 ++ lits2)
```

```
newtype Formula = Formula { ands :: [Ands]}
```

Introduction

Idea
Reversible
Superposition
Symbolic

Big Picture

Retrodictive

Examples

Software

Requirements

Design

Evaluation

Running
Timings
Complexity

Conclusion

Extras

Cost Models

Design

Second, using sets of ints and occurrence maps:

```

type Literal = Int
newtype Ands = Ands { lits :: IS.IntSet }

{-# INLINABLE compAnds #-}
compAnds :: Ands -> Ands -> Ordering
compAnds (Ands a1) (Ands a2) =
    compare (IS.toAscList a1) (IS.toAscList a2)

(&&&) :: Ands -> Ands -> Ands
(Ands lits1) &&& (Ands lits2) =
    Ands (IS.union lits1 lits2)

-- raw XOR formulas
type XORFU = Map.Map Ands Int
-- Normalized XOR formulas, i.e occur 0 or 1 time
newtype Formula = Formula { ands :: MS.MultiSet Ands }

```

Introduction

Idea

Reversible

Superposition

Symbolic

Big Picture

Retroductive

Examples

Software

Requirements

Design

Evaluation

Running

Timings

Complexity

Conclusion

Extras

Cost Models

Design

Third, using bitmaps and occurrence maps:

```
type Literal = Natural
newtype Ands = Ands { lits :: Literal }
```

```
{-# INLINABLE compAnds #-}
compAnds :: Ands -> Ands -> Ordering
compAnds (Ands a1) (Ands a2) = compare a1 a2
```

```
(&&&) :: Ands -> Ands -> Ands
(Ands lits1) &&& (Ands lits2) = Ands (lits1 .|. lits2)
```

```
type Occur = Int
-- Raw XOR formulas
type XORFU = Map.Map Ands Occur
-- Normalized XOR formulas, i.e occur 0 or 1 time
type XORF = MS.MultiSet Ands
```

Running Deutsch-Josza

- **Retrodictive once** on output measurement 0
- Output symbolic formula that decides $f(|\mathbf{x}\rangle) = 0$.
- f constant $\Rightarrow 0 = 0$ or $1 = 0$ regardless of circuit size.

Introduction

Idea
Reversible
Superposition
Symbolic

Big Picture

Retrodictive

Examples

Software

Requirements
Design

Evaluation

Running
Timings
Complexity

Conclusion

Extras

Cost Models

Running Deutsch-Josza

- **Retrodictive once** on output measurement 0
- Output symbolic formula that decides $f(|\mathbf{x}\rangle) = 0$.
- f constant $\Rightarrow 0 = 0$ or $1 = 0$ regardless of circuit size.

Sample outputs:

- $x_0 = 0$,
- $x_0 \oplus x_1 \oplus x_2 \oplus x_3 \oplus x_4 \oplus x_5 = 0$, and
- $1 \oplus x_3x_5 \oplus x_2x_4 \oplus x_1x_5 \oplus x_0x_3 \oplus x_0x_2 \oplus x_3x_4x_5 \oplus x_2x_3x_5 \oplus x_1x_3x_5 \oplus x_0x_3x_5 \oplus x_0x_1x_4 \oplus x_0x_1x_2 \oplus x_2x_3x_4x_5 \oplus x_1x_3x_4x_5 \oplus x_1x_2x_4x_5 \oplus x_1x_2x_3x_5 \oplus x_0x_3x_4x_5 \oplus x_0x_2x_4x_5 \oplus x_0x_2x_3x_5 \oplus x_0x_1x_4x_5 \oplus x_0x_1x_3x_5 \oplus x_0x_1x_3x_4 \oplus x_0x_1x_2x_4 \oplus x_0x_1x_2x_4x_5 \oplus x_0x_1x_2x_3x_5 \oplus x_0x_1x_2x_3x_4 = 0$.

How to decide? If it mentions a variable, it's balanced.

We tested all 12872 functions $\mathbb{B}^6 \rightarrow \mathbb{B}$.

Running Deutsch-Josza

- **Retrodictive once** on output measurement 0
- Output symbolic formula that decides $f(|\mathbf{x}\rangle) = 0$.
- f constant $\Rightarrow 0 = 0$ or $1 = 0$ regardless of circuit size.

Sample outputs:

- $x_0 = 0$,
- $x_0 \oplus x_1 \oplus x_2 \oplus x_3 \oplus x_4 \oplus x_5 = 0$, and
- $1 \oplus x_3x_5 \oplus x_2x_4 \oplus x_1x_5 \oplus x_0x_3 \oplus x_0x_2 \oplus x_3x_4x_5 \oplus x_2x_3x_5 \oplus x_1x_3x_5 \oplus x_0x_3x_5 \oplus x_0x_1x_4 \oplus x_0x_1x_2 \oplus x_2x_3x_4x_5 \oplus x_1x_3x_4x_5 \oplus x_1x_2x_4x_5 \oplus x_1x_2x_3x_5 \oplus x_0x_3x_4x_5 \oplus x_0x_2x_4x_5 \oplus x_0x_2x_3x_5 \oplus x_0x_1x_4x_5 \oplus x_0x_1x_3x_5 \oplus x_0x_1x_3x_4 \oplus x_0x_1x_2x_4 \oplus x_0x_1x_2x_4x_5 \oplus x_0x_1x_2x_3x_5 \oplus x_0x_1x_2x_3x_4 = 0$.

How to decide? If it mentions a variable, it's balanced.

We tested all 12872 functions $\mathbb{B}^6 \rightarrow \mathbb{B}$.

Introduction

Idea

Reversible

Superposition

Symbolic

Big Picture

Retrodictive

Examples

Software

Requirements

Design

Evaluation

Running

Timings

Complexity

Conclusion

Extras

Cost Models

Recall: guess the position of the single 1 bit.

$n = 4$, w in the range $\{0..15\}$

$u = 0$	$1 \oplus x_3 \oplus x_2 \oplus x_1 \oplus x_0 \oplus x_2x_3 \oplus x_1x_3 \oplus x_1x_2 \oplus x_0x_3 \oplus x_0x_2 \oplus x_0x_1 \oplus x_1x_2x_3 \oplus x_0x_2x_3 \oplus x_0x_1x_3 \oplus x_0x_1x_2 \oplus x_0x_1x_2x_3$
$u = 1$	$x_0 \oplus x_0x_3 \oplus x_0x_2 \oplus x_0x_1 \oplus x_0x_2x_3 \oplus x_0x_1x_3 \oplus x_0x_1x_2 \oplus x_0x_1x_2x_3$
$u = 2$	$x_1 \oplus x_1x_3 \oplus x_1x_2 \oplus x_0x_1 \oplus x_1x_2x_3 \oplus x_0x_1x_3 \oplus x_0x_1x_2 \oplus x_0x_1x_2x_3$
$u = 3$	$x_0x_1 \oplus x_0x_1x_3 \oplus x_0x_1x_2 \oplus x_0x_1x_2x_3$
$u = 4$	$x_2 \oplus x_2x_3 \oplus x_1x_2 \oplus x_0x_2 \oplus x_1x_2x_3 \oplus x_0x_2x_3 \oplus x_0x_1x_2 \oplus x_0x_1x_2x_3$
$u = 5$	$x_0x_2 \oplus x_0x_2x_3 \oplus x_0x_1x_2 \oplus x_0x_1x_2x_3$
$u = 6$	$x_1x_2 \oplus x_1x_2x_3 \oplus x_0x_1x_2 \oplus x_0x_1x_2x_3$
$u = 7$	$x_0x_1x_2 \oplus x_0x_1x_2x_3$
$u = 8$	$x_3 \oplus x_2x_3 \oplus x_1x_3 \oplus x_0x_3 \oplus x_1x_2x_3 \oplus x_0x_2x_3 \oplus x_0x_1x_3 \oplus x_0x_1x_2x_3$
$u = 9$	$x_0x_3 \oplus x_0x_2x_3 \oplus x_0x_1x_3 \oplus x_0x_1x_2x_3$
$u = 10$	$x_1x_3 \oplus x_1x_2x_3 \oplus x_0x_1x_3 \oplus x_0x_1x_2x_3$
$u = 11$	$x_0x_1x_3 \oplus x_0x_1x_2x_3$
$u = 12$	$x_2x_3 \oplus x_1x_2x_3 \oplus x_0x_2x_3 \oplus x_0x_1x_2x_3$
$u = 13$	$x_0x_2x_3 \oplus x_0x_1x_2x_3$
$u = 14$	$x_1x_2x_3 \oplus x_0x_1x_2x_3$
$u = 15$	$x_0x_1x_2x_3$

Problem

Factor a given N . Do this by using $f(x) = a^x \pmod N$ for suitable a and $f : \mathbb{B}^Q \rightarrow \mathbb{B}^n$ with $Q = \lceil \log_2(N^2) \rceil$, $n = \lceil \log_2 N \rceil$.

Factoring 15:

Base	Equations	Solution
$a = 11$	$x_0 = 0$	$x_0 = 0$
$a = 4, 14$	$1 \oplus x_0 = 1$	$x_0 = 0$
$a = 7, 13$	$1 \oplus x_1 \oplus x_0 x_1 = 1$	$x_0 = x_1 = 0$
$a = 2, 8$	$1 \oplus x_0 \oplus x_1 \oplus x_0 x_1 = 1$	$x_0 = x_1 = 0$

Auto-generated circuits: 56,538 generalized Toffoli gates.

Introduction

Idea

Reversible

Superposition

Symbolic

Big Picture

Retrodictive

Examples

Software

Requirements

Design

Evaluation

Running

Timings

Complexity

Conclusion

Extras

Cost Models

Problem

Factor a given N . Do this by using $f(x) = a^x \pmod N$ for suitable a and $f : \mathbb{B}^Q \rightarrow \mathbb{B}^n$ with $Q = \lceil \log_2(N^2) \rceil$, $n = \lceil \log_2 N \rceil$.

Factoring 15:

Base	Equations	Solution
$a = 11$	$x_0 = 0$	$x_0 = 0$
$a = 4, 14$	$1 \oplus x_0 = 1$	$x_0 = 0$
$a = 7, 13$	$1 \oplus x_1 \oplus x_0 x_1 = 1$	$x_0 = x_1 = 0$
$a = 2, 8$	$1 \oplus x_0 \oplus x_1 \oplus x_0 x_1 = 1$	$x_0 = x_1 = 0$

Auto-generated circuits: 56,538 generalized Toffoli gates.

For $3 \cdot 65537 = 196611$ (4,328,778 gates), 16 small equations that refer to just the four variables $x_0, x_1, x_2,$ and x_3 constraining them to be all 0, i.e., asserting that the period is 16.

Timings: Deutsch-Jozsa

 


Figure: Retrodictive execution on 3 balanced functions at different sizes

Introduction

- Idea
- Reversible
- Superposition
- Symbolic

Big Picture

- Retrodictive

Examples

Software

- Requirements
- Design

Evaluation

- Running
- Timings**
- Complexity

Conclusion

Extras

- Cost Models

Timings: Grover on different values

 


Figure: Retrodictive execution of the Grover algorithm on different “secret” values u at different sizes

Timings: Grover with different representations

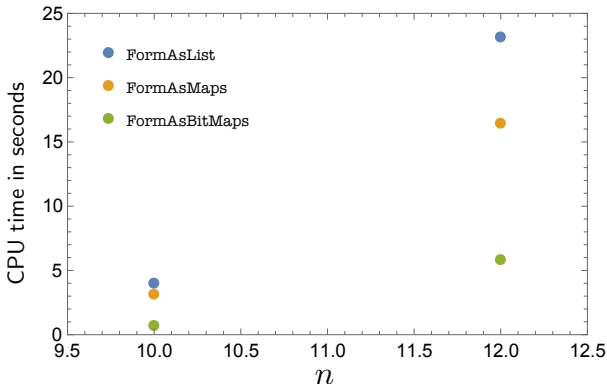


Figure: Retrodective execution of the Grover algorithm on secret value $u = 0$ at two sizes but using different ANF representations

Introduction

Idea
Reversible
Superposition
Symbolic

Big Picture

Retrodective

Examples

Software

Requirements
Design

Evaluation

Running
Timings
Complexity

Conclusion

Extras

Cost Models

Complexity

Problem: circuit with T generalized Toffoli gates over $n + m$ qubits split into two registers (A, B) .

- ① Design oracle / circuit.
- ② Let $A = |00 \dots 0\rangle$ and $B = |00 \dots 0\rangle$ and run classically. $\mathcal{O}(T)$. Leaves A intact, produce b in B .
- ③ Run backwards (symbolically) with $A = |x_{n-1} \dots x_1 x_0\rangle$ and $B = |b\rangle$. Worst case, equations sized $\mathcal{O}(2^n)$, so $\mathcal{O}(Tm2^n)$.
- ④ Answer by inspecting/solving resulting m equations.

Introduction

Idea

Reversible

Superposition

Symbolic

Big Picture

Retrodictive

Examples

Software

Requirements

Design

Evaluation

Running

Timings

Complexity

Conclusion

Extras

Cost Models

Complexity

Problem: circuit with T generalized Toffoli gates over $n + m$ qubits split into two registers (A, B) .

- ① Design oracle / circuit.
- ② Let $A = |00 \dots 0\rangle$ and $B = |00 \dots 0\rangle$ and run classically. $\mathcal{O}(T)$. Leaves A intact, produce b in B .
- ③ Run backwards (symbolically) with $A = |x_{n-1} \dots x_1 x_0\rangle$ and $B = |b\rangle$. Worst case, equations sized $\mathcal{O}(2^n)$, so $\mathcal{O}(Tm2^n)$.
- ④ Answer by inspecting/solving resulting m equations.

Bottlenecks:

- step (3) at worst case $\mathcal{O}(Tm2^n)$,
- step (4) “solve”, which is NP -complete.

However:

- Sometimes ‘typical’ case has expected run-time depending on bit-size of the information contained in the answer.

Conclusion

- Different algorithms **need** different analyses to extract answer.
- (Not shown in slides) Shor seems to need qutrits/qudits in general.
- For a number of classical **quantum** algorithms, classical but **symbolic** execution works just as well.
- Even better: symbolic execute **once** instead of “enough” times to get probabilistic answer.
- Symbolic execution sometimes is **really bad**.

Introduction

Idea
Reversible
Superposition
Symbolic

Big Picture

Retrodictive

Examples

Software

Requirements
Design

Evaluation

Running
Timings
Complexity

Conclusion

Extras

Cost Models

Conclusion

- Different algorithms **need** different analyses to extract answer.
- (Not shown in slides) Shor seems to need qutrits/qudits in general.
- For a number of classical **quantum** algorithms, classical but **symbolic** execution works just as well.
- Even better: symbolic execute **once** instead of “enough” times to get probabilistic answer.
- Symbolic execution sometimes is **really bad**.
- **Speculation**: some common quantum algorithms might not need quantum after all.

Introduction

Idea

Reversible

Superposition

Symbolic

Big Picture

Retrodictive

Examples

Software

Requirements

Design

Evaluation

Running

Timings

Complexity

Conclusion

Extras

Cost Models

Introduction

Idea

Reversible

Superposition

Symbolic

Big Picture

Retrodictive

Examples

Software

Requirements

Design

Evaluation

Running

Timings

Complexity

Conclusion

Extras

Cost Models

- White-box model: *We* implement U_f and the cost of implementing it and the cost of using it is counted as part of the overall complexity
- Black-box model: “Someone” implements U_f and gives us access to it; the complexity analysis only counts the number of times U_f is used. There are different cases based on what kind of access we are given:
 - Query U_f on a classical input
 - Query U_f on a quantum superposition
 - Query U_f on a *symbolic formula* (**NEW!**)